

OSMANIA UNIVERSITY
FACULTY OF ENGINEERING
UNIVERSITY COLLEGE OF ENGINEERING (AUTONOMOUS)
B.E. (ECE, BME, CSE, AI&ML) I-Semester (MAIN) Examinations JAN/FEB-2025

BASIC ELECTRICAL ENGINEERING

Time : 3 hours

Max. Marks : 60

- Note : i) Answer *Question No. 1* (Compulsory) and answer any *four* questions from the remaining questions (2- 7). Each question carries 12 marks.
ii) Answers must be written in same order as they occur in the Question Paper.
iii) Missing data, if any may suitably be assumed.

	Marks	BT	CO
1. a) Compute the equivalent resistance of three resistors connected in parallel.	2	1	1
b) Define form factor and peak factor.	2	1	2
c) Differentiate between ideal and practical transformer.	2	3	3
d) State Fleming's rules.	2	1	4
e) What is the difference between MCB and MCCB.	2	3	5
f) Define power factor.	2	1	5
2. a) State and explain Superposition theorem with an example.	6	2	1
b) A Wheatstone bridge ABCD is arranged as follows: $AB = 10\Omega$, $BC = 30\Omega$, $CD = 15\Omega$ and $DA = 20\Omega$. A 2 volt battery of internal resistance 2Ω is connected between A and C with A positive. A galvanometer of resistance 40Ω is connected between B and D. Find the magnitude and direction of current through galvanometer using Kirchhoff's laws.	6	3	1
3. a) Derive the relation between phase and line values of 3-phase balanced star connected load.	6	3	2
b) A series circuit has $R = 10\Omega$, $L = 50\text{ mH}$ and $C = 100\text{ }\mu\text{F}$ and is supplied with 200 V, 50 Hz. Find (i) Impedance, (ii) Current (iii) Power (iv) Power factor and (v) voltage drop across each element.	6	3	2

- | | | | | |
|-------|---|----|---|---|
| 4. a) | Explain how rotating magnetic field is produced in a 3-phase Induction motor. | 7 | 2 | 3 |
| b) | A 6600/440 V, 1-phase 600 kVA transformer has 1200 primary turns. Find (i) transformation ratio (ii) secondary turns (iii) voltage per turn (iv) secondary current when it supplies a load of 400 kW at 0.8 pf lagging. | 5 | 3 | 3 |
| 5. | With the aid of neat sketches, classify DC Generators. Mark the current directions and give the equations for the terminal voltage, generated emf and power developed in the armature. | 12 | 2 | 4 |
| 6. a) | What is the purpose of earthing. Explain any one type of earthing process. | 6 | 2 | 5 |
| b) | Explain the working of MCCB with the help of a neat sketch. | 6 | 2 | 5 |
| 7. a) | Draw the power triangle and explain the various types of powers. | 6 | 2 | 1 |
| b) | Explain the working of practical transformer with inductive load connected on the secondary side, draw the phasor diagram. | 6 | 2 | 3 |
